

Circuits

SEC (5)

First Order Circuits

* RC Circuits

$$\rightarrow v_c(t) = V(\infty) + (V(0) - V(\infty)) e^{-t/\tau} \quad V$$

$$\rightarrow i_c(t) = C \frac{dv_c(t)}{dt} \quad A$$

$$\rightarrow \tau = \underbrace{R_{\text{equiv}}}_{\substack{\text{seen} \\ \text{by the capacitor}}} \cdot C_{\text{equiv}} \quad \text{"sec"}$$

* RL Circuits

$$\rightarrow i_L(t) = I(\infty) + (I(0) - I(\infty)) e^{-t/\tau} \quad A$$

$$\rightarrow v_L(t) = L \frac{di_L(t)}{dt} \quad V$$

$$\rightarrow \tau = \frac{L_{\text{equiv}}}{\underbrace{R_{\text{equiv}}}_{\substack{\text{seen} \\ \text{by the inductor}}}} \quad \text{sec.}$$

(10)


SHEET (2)

For $t < 0$

$$\therefore i_{40\text{mH}}(0^-) = \frac{75}{5} = 15\text{ A} = i_{40\text{mH}}(0^+)$$

For $t > 0$

* Using source transformation (2 times).

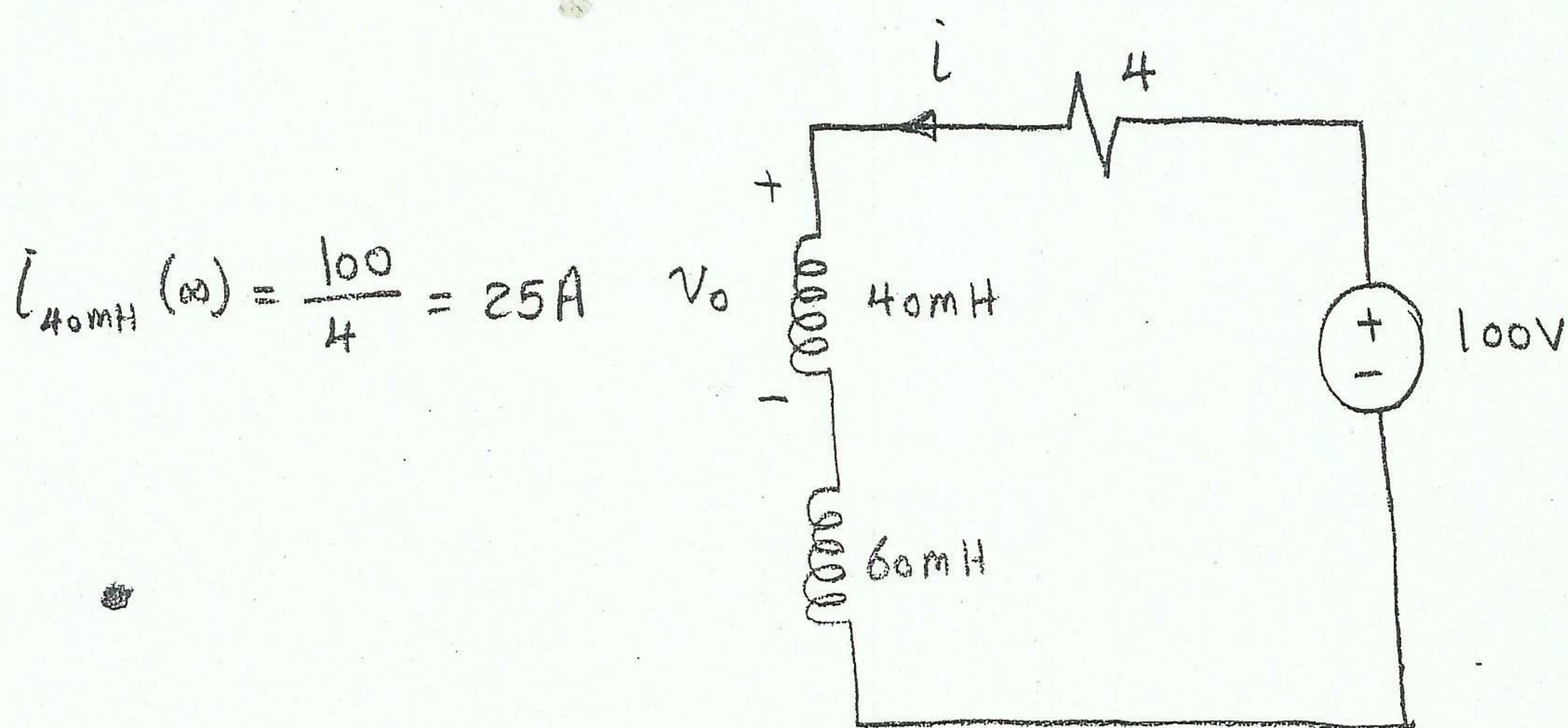

$$\therefore \tau = \frac{L_{\text{equiv}}}{R_{\text{equiv}}} = \frac{100\text{ mH}}{4} = 0.025\text{ s} \quad \left| \quad \frac{1}{\tau} = 40\text{ s}^{-1} \right.$$


$$\therefore \hat{i}(t) = 25 + (15 - 25)e^{-40t}$$

$$\therefore i(t) = 25 - 10e^{-40t}, \quad t \geq 0$$

$$\therefore v_o(t) = 0.04 \frac{di(t)}{dt} = 16e^{-40t}\text{ V}, \quad t \geq 0$$

(11)


$t < 0$

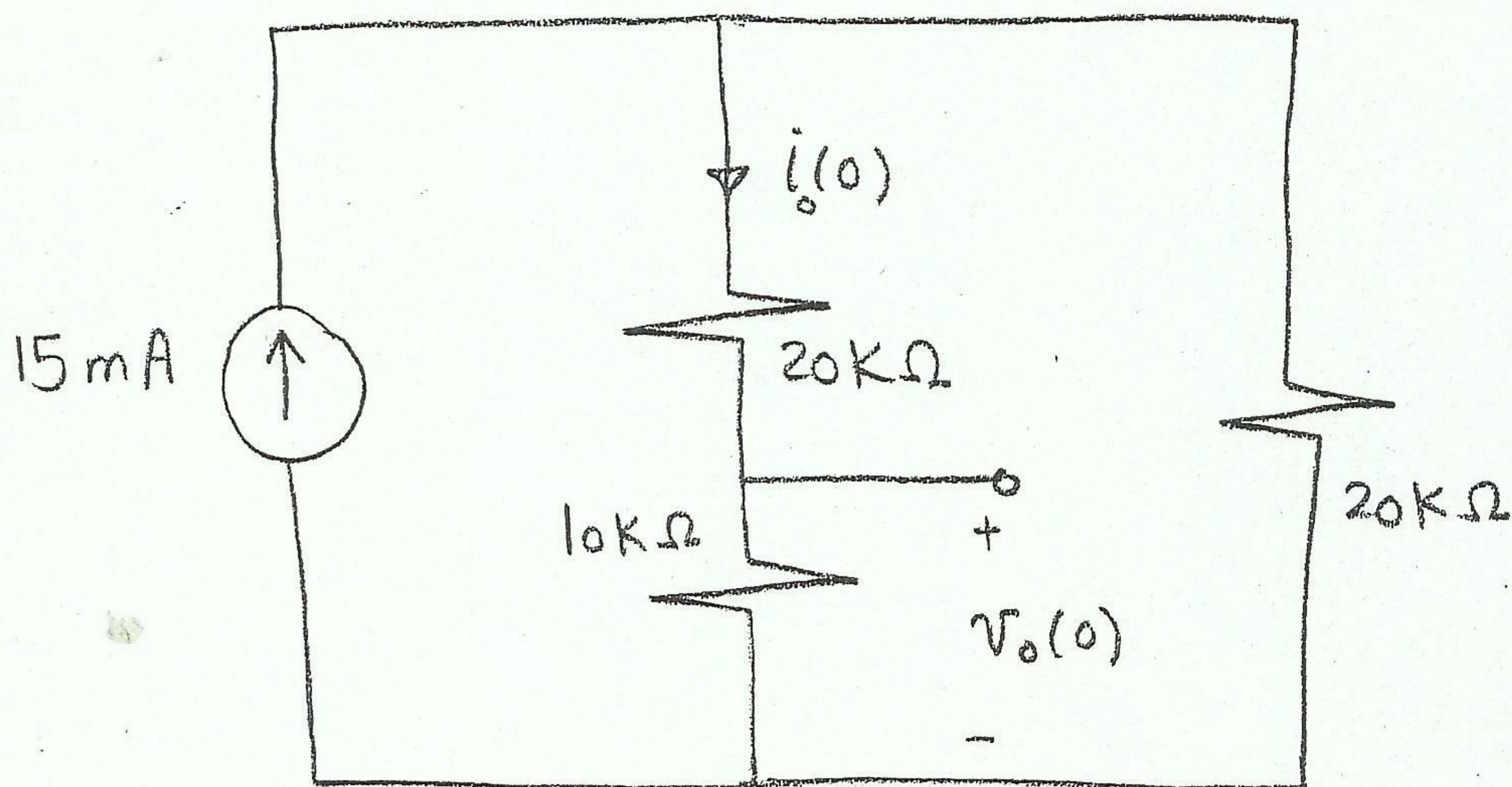

$$i_o(0) = 15\text{ mA} \times \frac{20}{20+30} = 6\text{ mA}$$

$$\therefore V_o(0) = 6 \times 10 = 60\text{ V}$$

$0 \leq t < \infty$

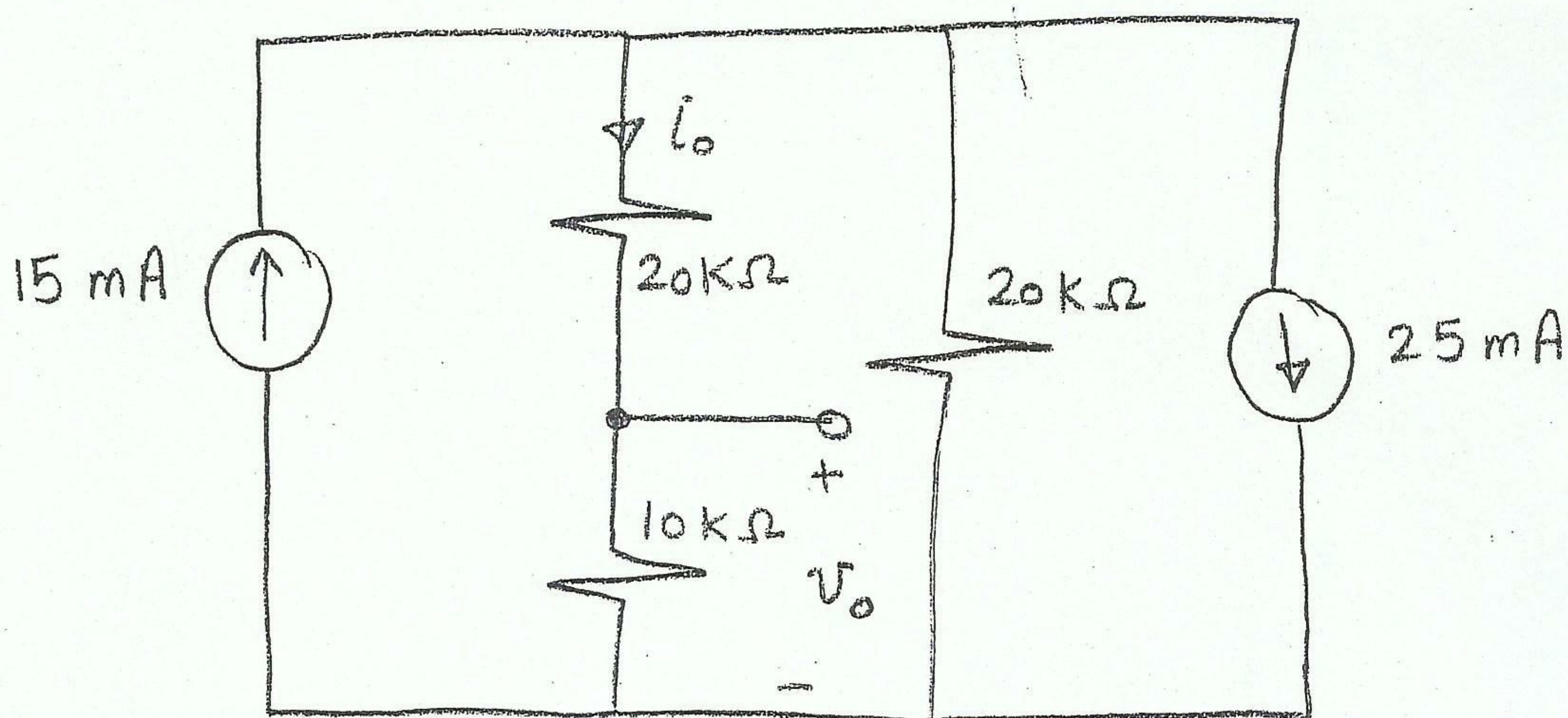

$$\therefore i_o(\infty) = -10\text{ mA} \times \frac{20}{20+30} = -4\text{ mA}$$


$$\therefore V_o(\infty) = -4 \times 10 = -40\text{ V}$$

$$R_{Th} = 10^k // (20^k + 20^k)$$


$$\therefore R_{Th} = 8 \text{ K}\Omega$$

$$\therefore \tau = 8 \text{ K} * 125 \text{ nF} = 1 \text{ ms}$$
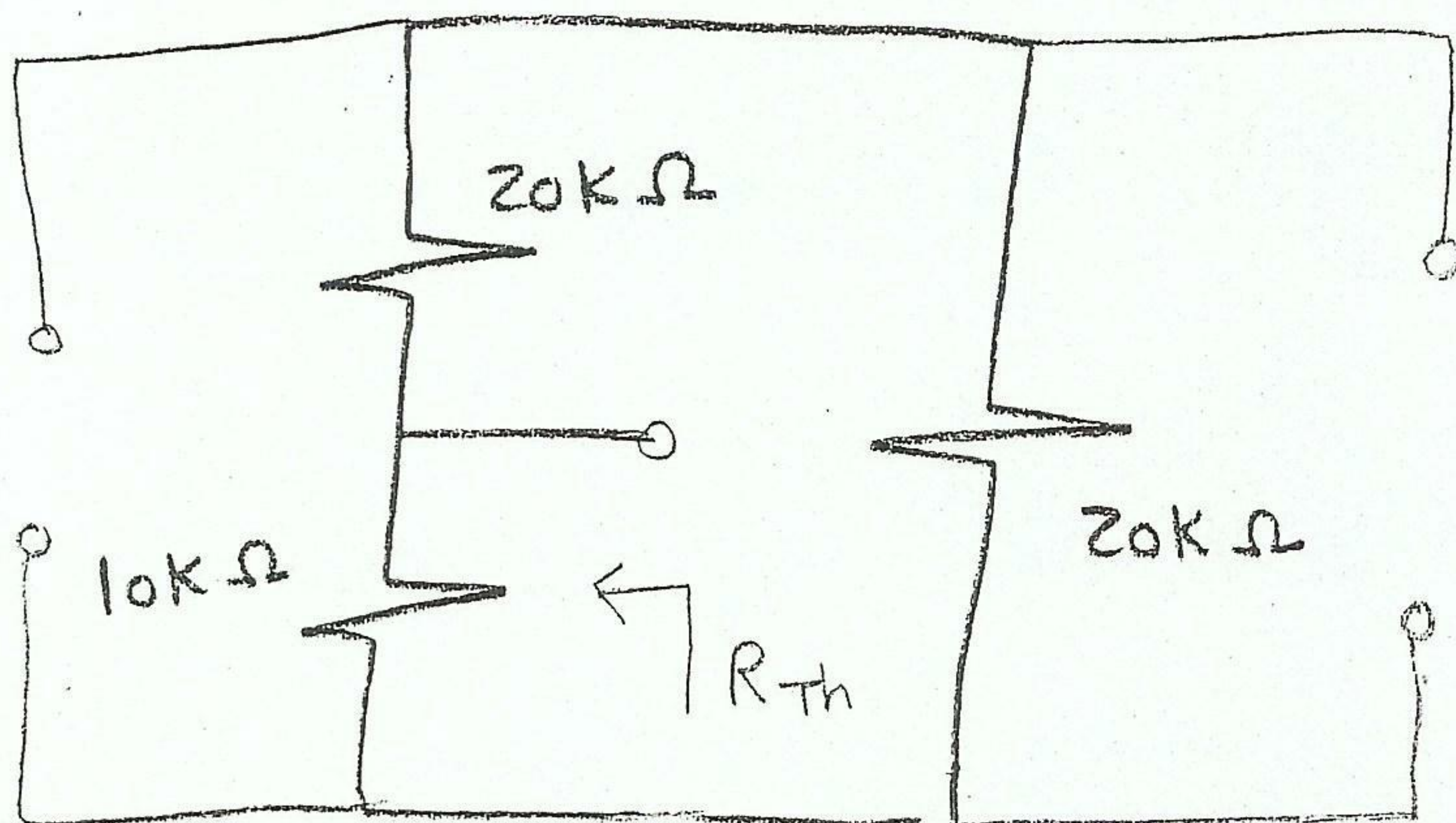
$$\therefore \frac{1}{\tau} = 1000 \text{ s}^{-1}$$


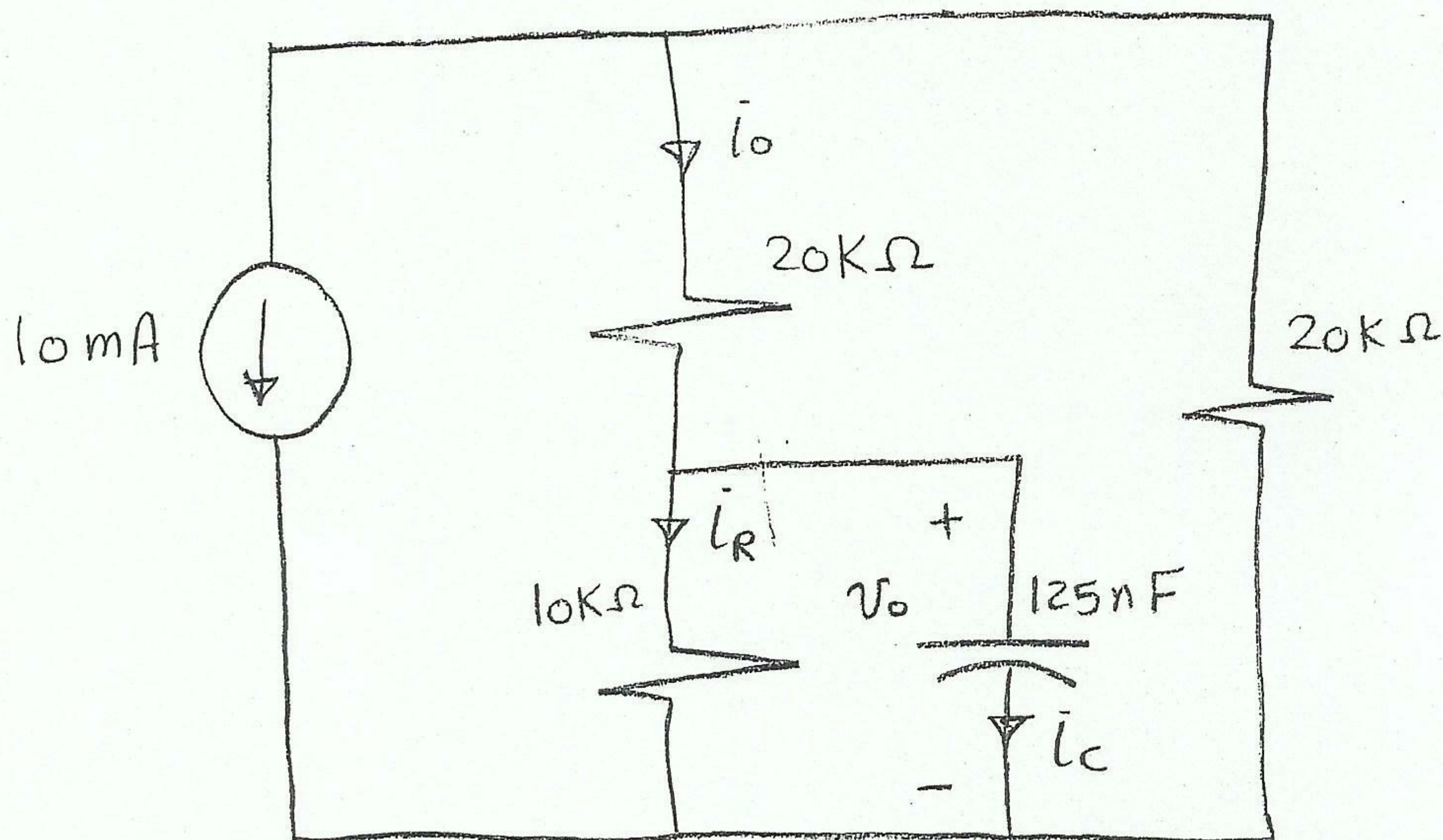
$$\therefore v_o(t) = -40 + 100 e^{-1000t} \text{ V}, t \geq 0^+$$



$$\therefore i_C = C \frac{dv}{dt}$$

$$\therefore i_C = -12.5 e^{-1000t} \text{ mA}$$

$$\therefore i_R = \frac{v_o(t)}{10 \text{ K}\Omega} = -4 + 10 e^{-1000t} \text{ mA}$$


$$\therefore i_o = i_C + i_R = -(4 + 2.5 e^{-1000t}) \text{ mA}, t \geq 0^+$$

(12.)

For $t < 0$

$$\dot{i}_b = 0 \quad (\text{short cct}) \quad \therefore V_c(\bar{0}) = 0$$

For $t > 0$

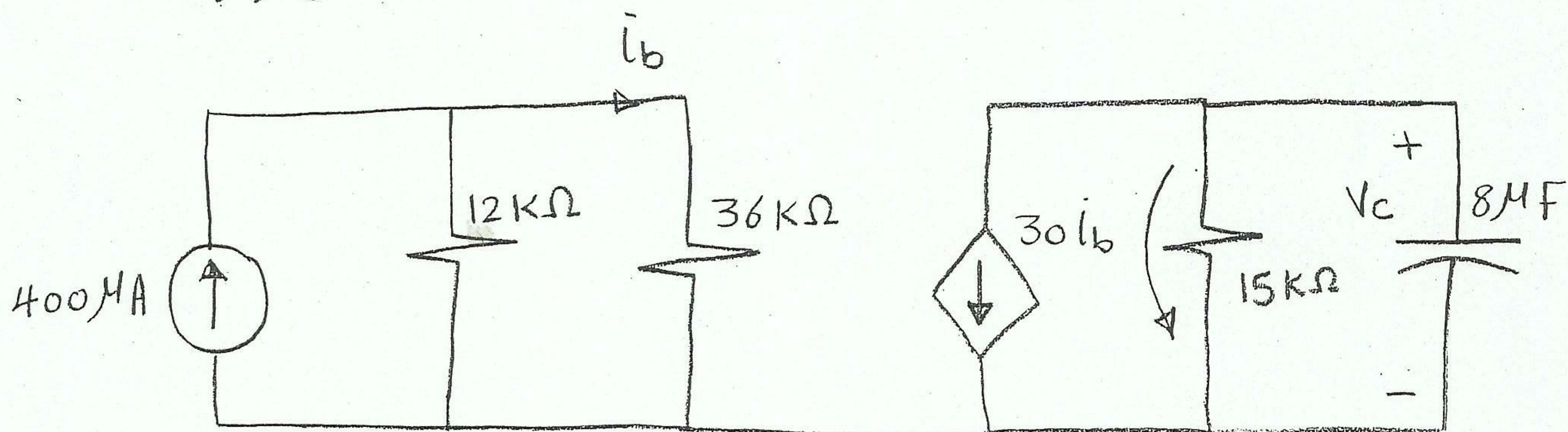

$$\therefore \dot{i}_b = 400 \mu A * \frac{12}{12 + 36} = 100 \mu A$$

$$\therefore V_c(\infty) = -30 \dot{i}_b * 15 k\Omega = -30 * 100 * 10^{-6} * 15 * 10^3$$

$$\therefore V_c(\infty) = -45 V$$


$$* R_{Th} = \frac{V_{Th}}{I_n} = \frac{V_{o.c}}{I_{s.c}}$$

$$\therefore V_{o.c} = -45 V, \quad I_{s.c} = -30 \dot{i}_b = -3 mA$$

$$\therefore R_{Th} = \frac{-45}{-0.003} = 15 k\Omega$$

$$\therefore \tau = 15 k * 8 \mu F = 120 ms$$

$$\therefore \frac{1}{\tau} = 8.33$$

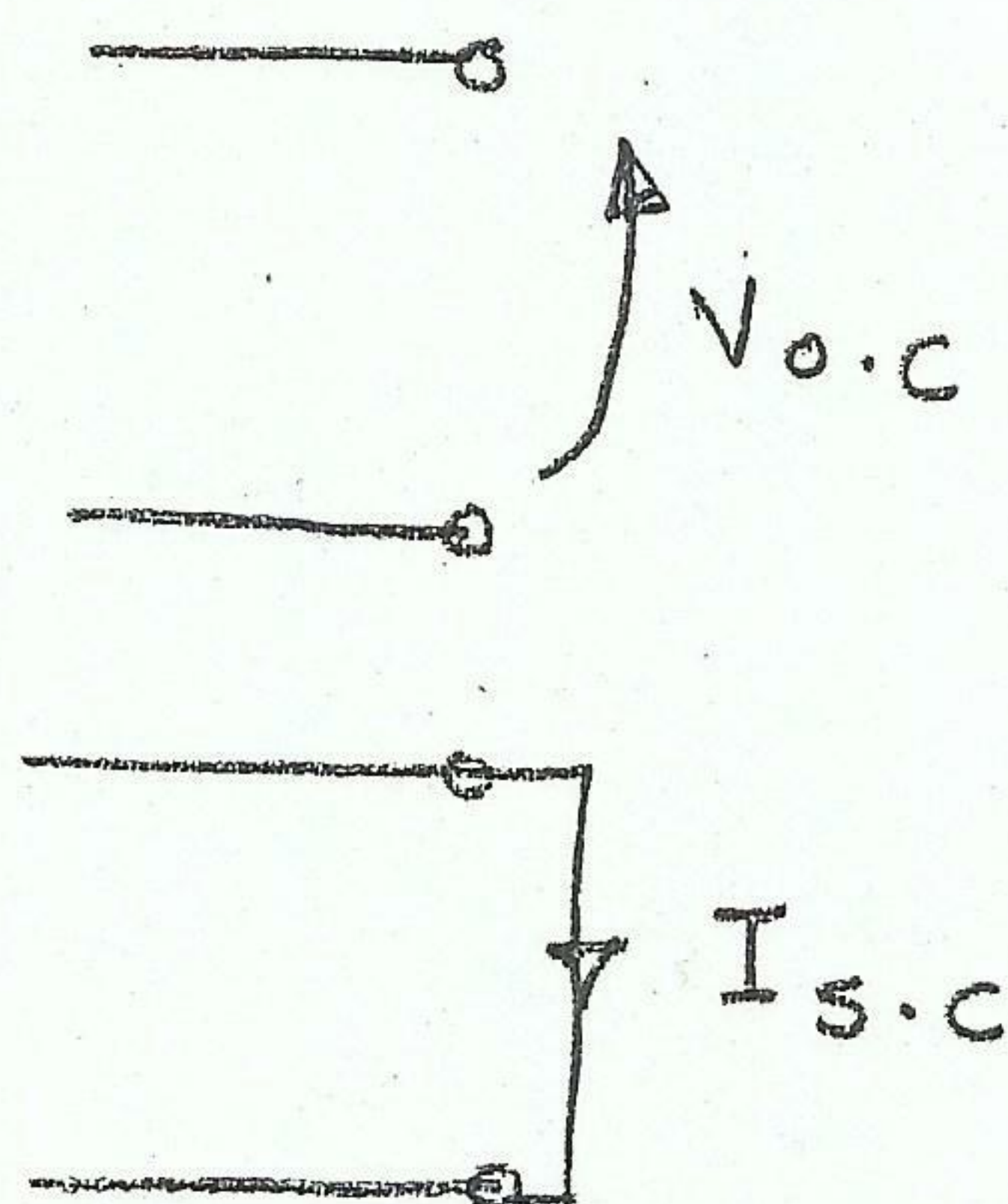

$$\therefore v_c(t) = -45 + (0 - (-45)) e^{-8.33t}$$

$$\therefore v_c(t) = -45 (1 - e^{-8.33t}), t \geq 0$$

$$\therefore W(t) = \frac{1}{2} C v_c^2(t) = \frac{1}{2} \times 8 \times 10^{-6} \times v_c^2(t)$$

$$\therefore W(t) = 8100 (1 - 2e^{-8.33t} + e^{-16.67t}) \text{ MJ}$$

$$\therefore W(\infty) = 8100 \text{ MJ}$$

$$\therefore 8100 (1 - 2e^{-8.33t} + e^{-16.67t}) = 0.9 \times 8100$$

$$\text{let } x = e^{-8.33t}$$

$$\therefore 1 - 2x + x^2 = 0.9$$

$$\therefore x = 1.9487, 0.0513$$

$$\therefore e^{-8.33t} = 0.0513$$

$$\therefore t = 356.4 \text{ ms}$$


(13)

$$(a) \quad L_{\text{equiv}} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} = \frac{0.125 - 0.0625}{0.75 + 0.5} = 50 \text{ mH}$$

$$\tau = \frac{L}{R} = \frac{1}{5000} \text{ s} \quad , \quad \frac{1}{\tau} = 5000 \text{ s}^{-1}$$

$$\therefore i_0(0) = 0 \quad , \quad i_0(\infty) = \frac{10}{250} = 40 \text{ mA}$$
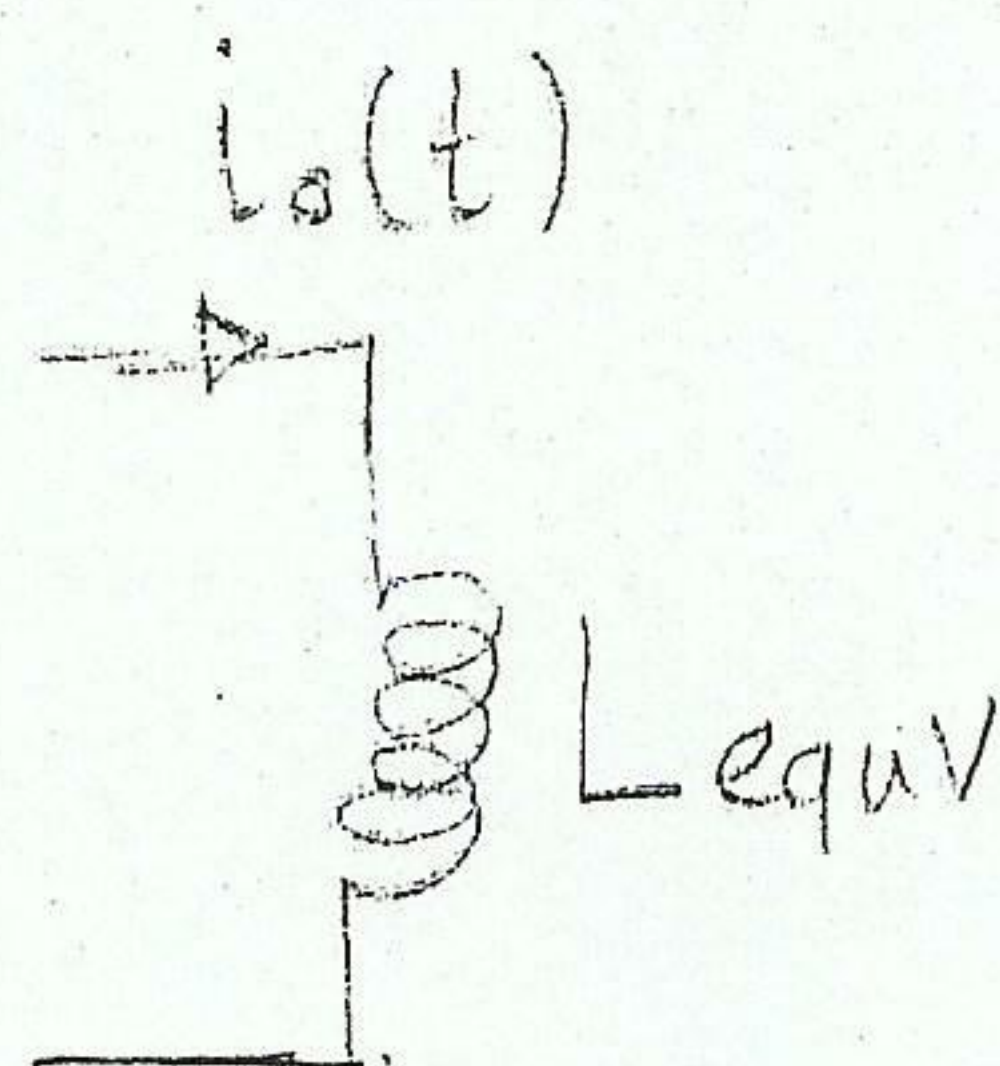
$$\therefore i_0(t) = 40 (1 - e^{-5000t}) \text{ mA}$$



$$(b) \quad V_0 = 10 - 250 i_0 = 10 - 250 \times \frac{40}{1000} (1 - e^{-5000t})$$

$$\therefore V_0(t) = 10 e^{-5000t} \text{ V} \quad \text{or} \quad V_0(t) = L_{\text{equiv}} \frac{di_0(t)}{dt}$$

$$(c) \quad \therefore V_0 = V_{L_1} = 0.5 \frac{di_1}{dt} - 0.25 \frac{di_2}{dt} = 10 e^{-5000t}$$

$$\therefore i_0 = i_1 + i_2$$

$$\therefore \frac{di_0}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt} = 200 e^{-5000t}$$

$$\therefore \frac{di_2}{dt} = 200 e^{-5000t} - \frac{di_1}{dt}$$

$$\therefore 10 e^{-5000t} = 0.5 \frac{di_1}{dt} - 50 e^{-5000t} + 0.25 \frac{di_1}{dt}$$

$$\therefore 0.75 \frac{di_1}{dt} = 60 e^{-5000t}$$

$$\therefore di_1 = 80 e^{-5000t} dt$$

$$\therefore i_1 = 80 \int_0^t e^{-5000t} dt$$

$$\therefore i_1(t) = 16 (1 - e^{-5000t}) \text{ mA}, t \geq 0$$

$$(d) \therefore i_2 = i_0 - i_1 = [40 (1 - e^{-5000t})] - [16 (1 - e^{-5000t})]$$

$$\therefore i_2(t) = 24 (1 - e^{-5000t}) \text{ mA}, t \geq 0$$

(14)

$$(a) \quad L_{\text{equiv}} = 4 + 8 - 2 \times 5 = 2 \text{ H}$$

$$\tau = \frac{L}{R} = \frac{2}{50} = \frac{1}{25} \text{ s} \quad \therefore \frac{1}{\tau} = 25 \text{ s}^{-1}$$

$$\therefore i(0) = 0, \quad \therefore i(\infty) = \frac{200}{50} = 4 \text{ A}$$

$$\therefore i(t) = 4 (1 - e^{-25t}) \text{ A}$$

$$(b) \quad v_1(t) = 4 \frac{di}{dt} - 5 \frac{di}{dt} = - \frac{di}{dt}$$


$$\therefore v_1(t) = -100 e^{-25t} \text{ V}, \quad t \geq 0^+$$

$$(c) \quad v_2(t) = 8 \frac{di}{dt} - 5 \frac{di}{dt} = 3 \frac{di}{dt}$$

$$\therefore v_2(t) = 300 e^{-25t}, \quad t \geq 0^+$$

(15)

For $t < 0$

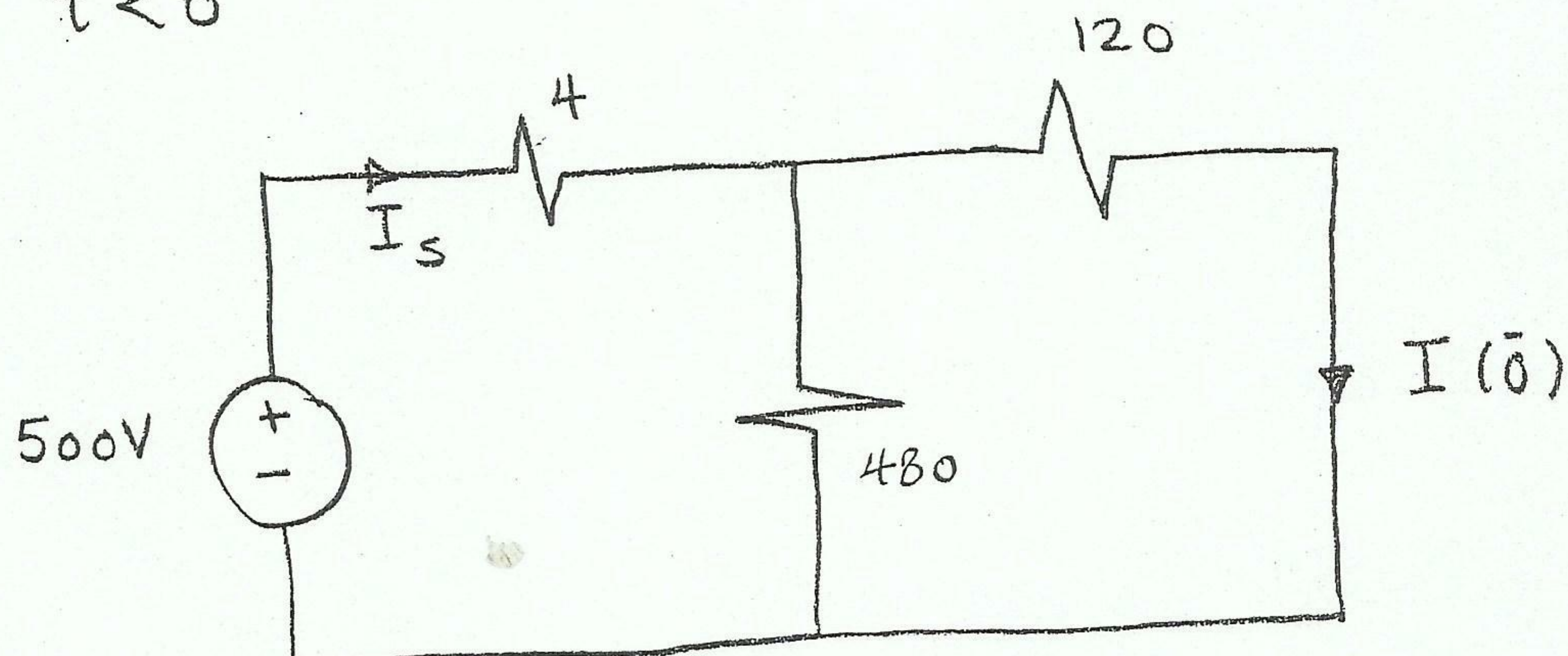

$$I_s = \frac{500}{4 + (120 // 480)} = 5A$$

$$\therefore I(0^-) = 5 \times \frac{480}{480 + 120} = 4A = I(0^+)$$

For $0 \leq t \leq 100 \mu s$


$$i(t) = 4 e^{-t/\tau}$$

$$R_{Th} = (96 // 480) + 120$$

$$\therefore R_{Th} = 200 \Omega$$

$$\therefore \frac{1}{\tau} = \frac{R}{L} = \frac{200}{0.02} = 10,000 \text{ s}^{-1}$$


$$\therefore i(t) = 4 e^{-10,000 t}$$

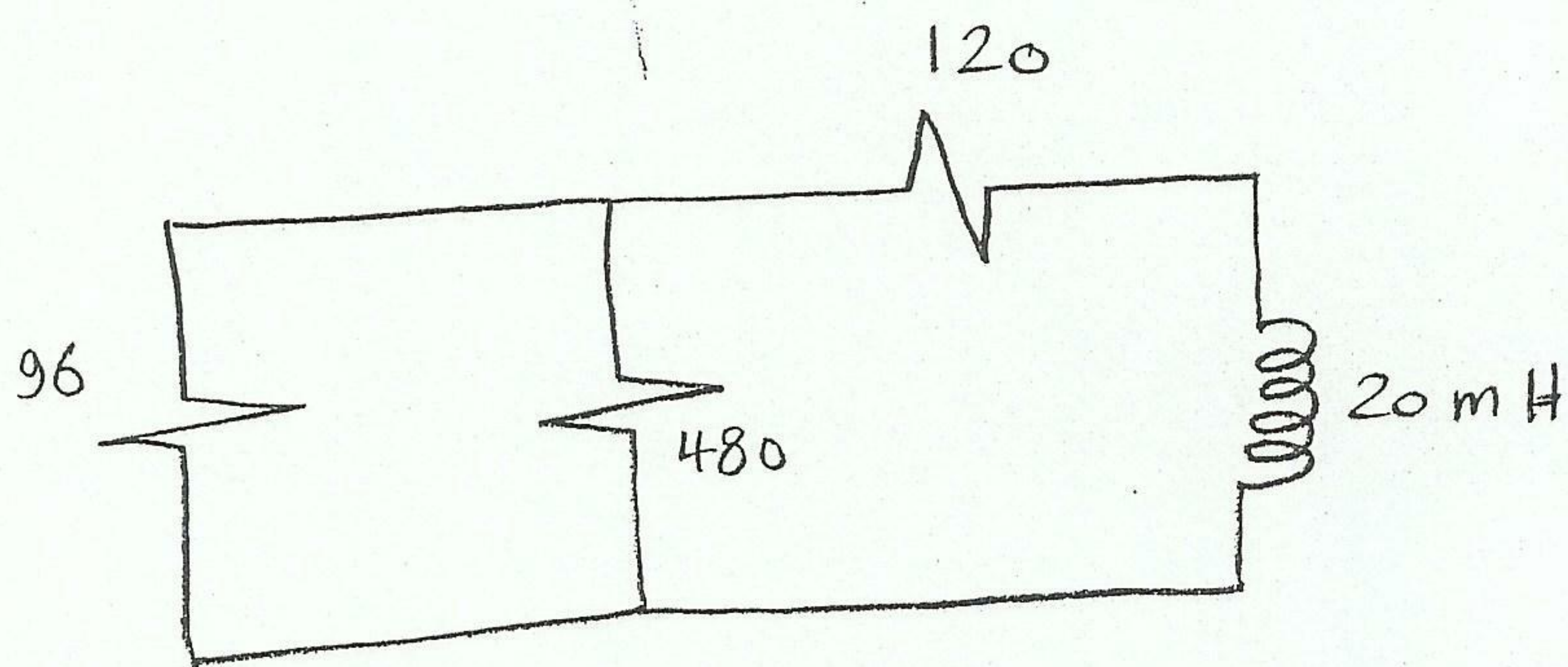

$$\therefore i(25 \mu s) = 4 e^{-10^4 \times 25 \times 10^{-6}} = 3.12 A$$

$$\therefore \dot{i}(100\mu s) = 4 e^{-10^4 * 10^{-4}} = 4 e^{-1} = 1.47 \text{ A}$$

For $100\mu s \leq t < \infty$

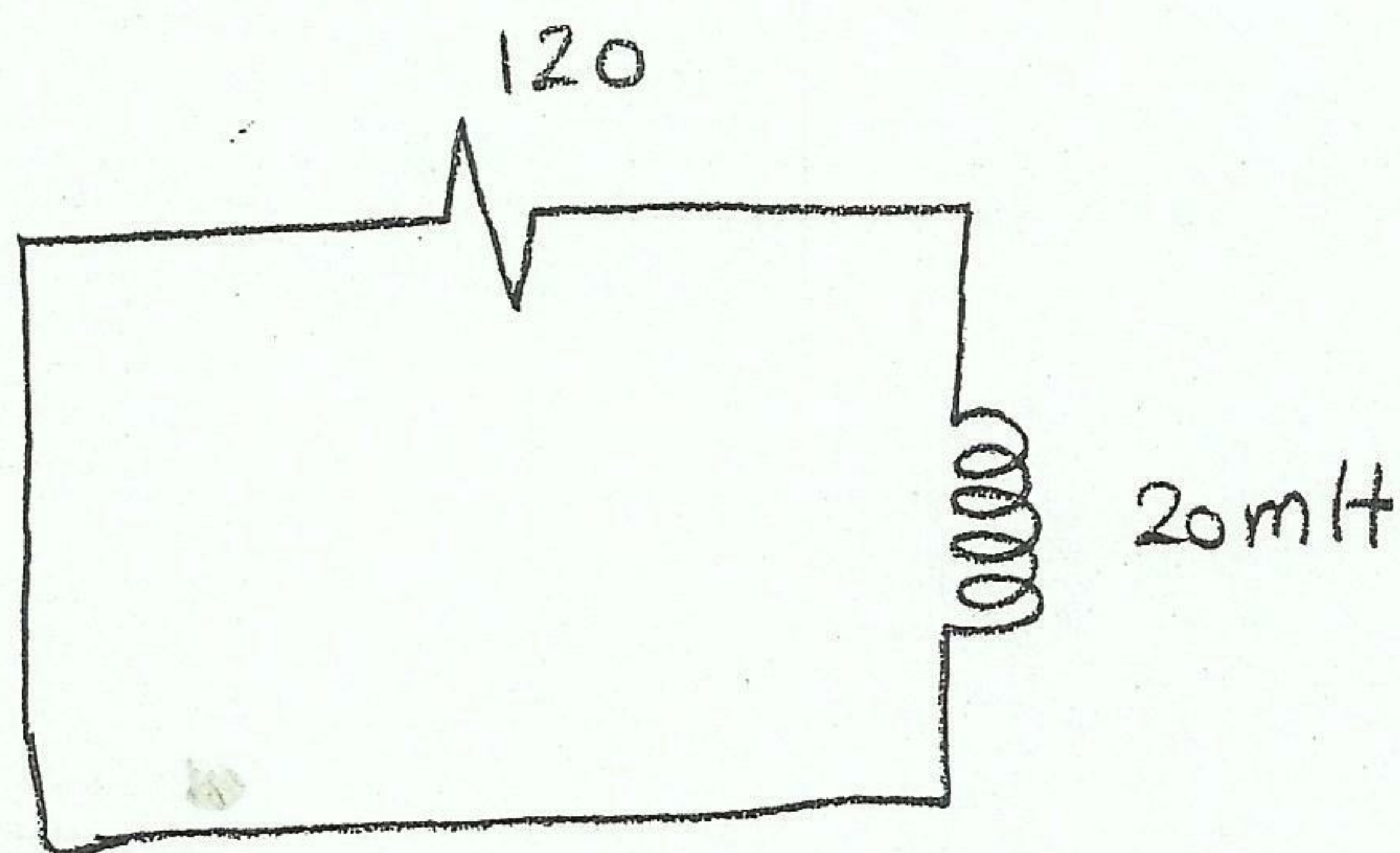

$$\frac{1}{\tau} = \frac{R}{L} = \frac{120}{0.02} = 6000 \text{ s}^{-1}$$

$$\therefore \dot{i}(t) = 1.47 e^{-6000t} \text{ A}$$

$$\therefore \dot{i}(200\mu s) = 1.47 e^{-6 \times 10^3 * 200 \times 10^{-6}} = 1.47 e^{-0.6}$$

$$\therefore \dot{i}(200\mu s) = 807.59 \text{ mA}$$

When $0 \leq t \leq 100\mu s$

$$\therefore \dot{i}(t) = 4 e^{-10,000t}$$

$$\therefore v_L(t) = L \frac{di}{dt} = 0.02 * 4 * -10^4 e^{-10^4 t}$$

$$\therefore v_L(t) = -800 e^{-10^4 t} \text{ V}$$

$$\therefore v_L(100\mu s) = -800 * e^{-10^4 * 10^{-4}} = -800 e^{-1}$$

$$\therefore v_L(100\mu s) = -294.3 \text{ V}$$

When

$$100 \mu s \leq t < \infty$$

$$= i(t) = 1.47 e^{-6000(t - 100 \times 10^{-6})}$$

$$\therefore V_L = 0.02 * 1.47 * (-6000) e^{-6000(t - 100 \times 10^{-6})}$$

$$\therefore V_L(t) = -176.58 e^{-6000(t - 10^{-4})} \text{ V}$$


$$\therefore V_L(100^+ \mu s) = -176.58 e^{-600(10^{-4} - 10^{-4})}$$

$$\therefore V_L(100^+ \mu s) = -176.58 \text{ V}$$

(16)


For $t < 0$

* Using Source Transformation:

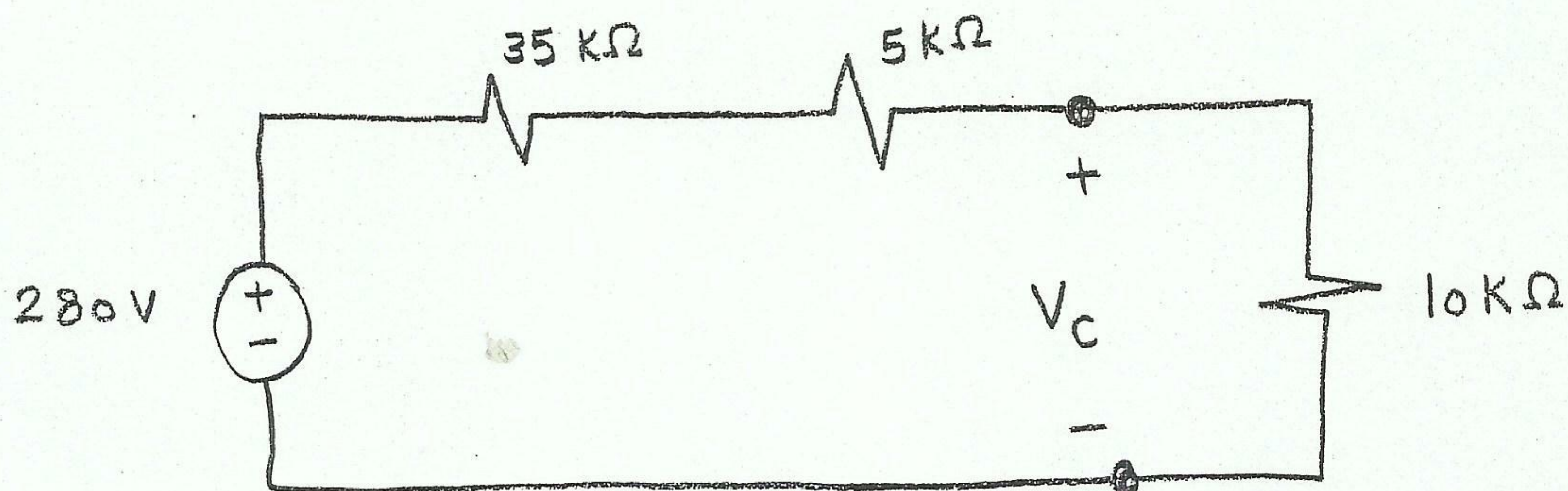

$$\therefore V_c(0) = 280 \times \frac{10}{10 + 40} = 56\text{ V}$$

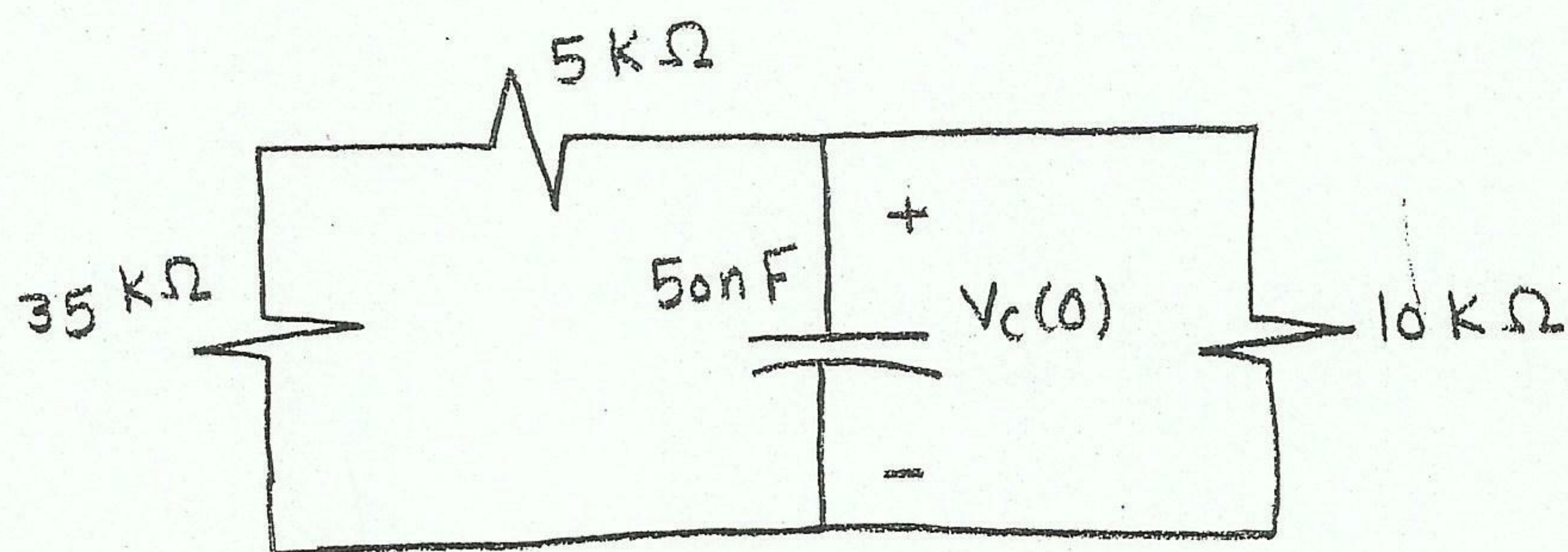For $0 \leq t \leq 400\text{ }\mu\text{s}$




$$\tau = R_{Th} * C, \quad R_{Th} = (5 + 35) // 10 = 8\text{ k}\Omega$$

$$\therefore \tau = 8 \times 10^3 * 50 \times 10^{-9} = 400\text{ }\mu\text{s}$$

$$\therefore V_c(t) = 56 e^{-t/\tau}$$

$$\therefore V_c(400\text{ }\mu\text{s}) = 56 * e^{-1} = 20.6\text{ V}$$

For $400 \mu s < t < 1.4 \text{ ms}$

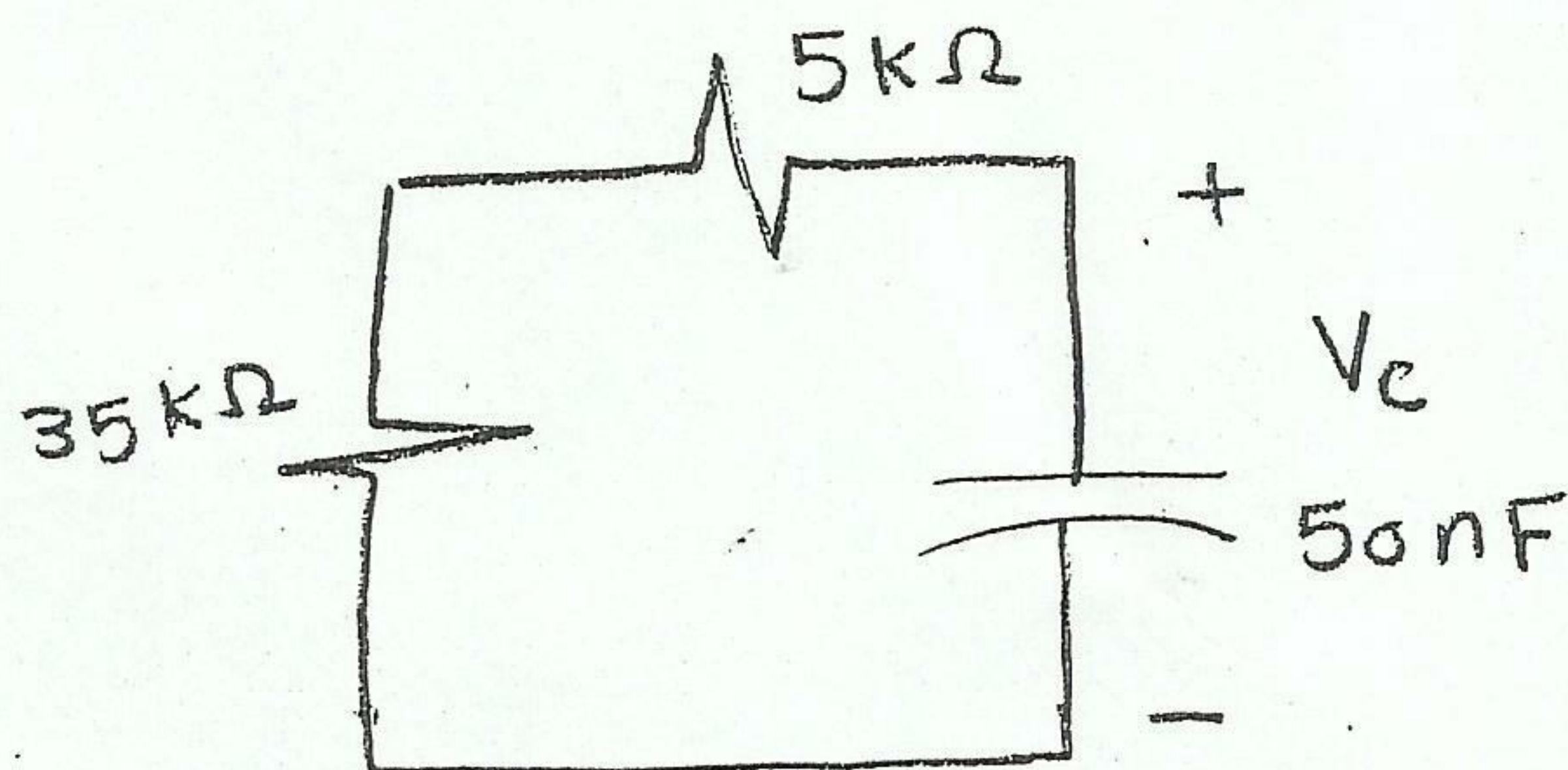


$$\tau = (40 \text{ k}\Omega) \cdot (50 \text{ nF}) = 2 \text{ ms} \quad , \quad \frac{1}{\tau} = 500 \text{ s}^{-1}$$

$$\therefore V_c(t) = 20.6 e^{-500(t - 400 \times 10^{-6})} \text{ V}$$

$$\therefore V_c(1.4 \text{ ms}) = 20.6 e^{-500(1400 - 400) \times 10^{-6}} = 12.5 \text{ V}$$

For $1.4 \text{ ms} < t < \infty$

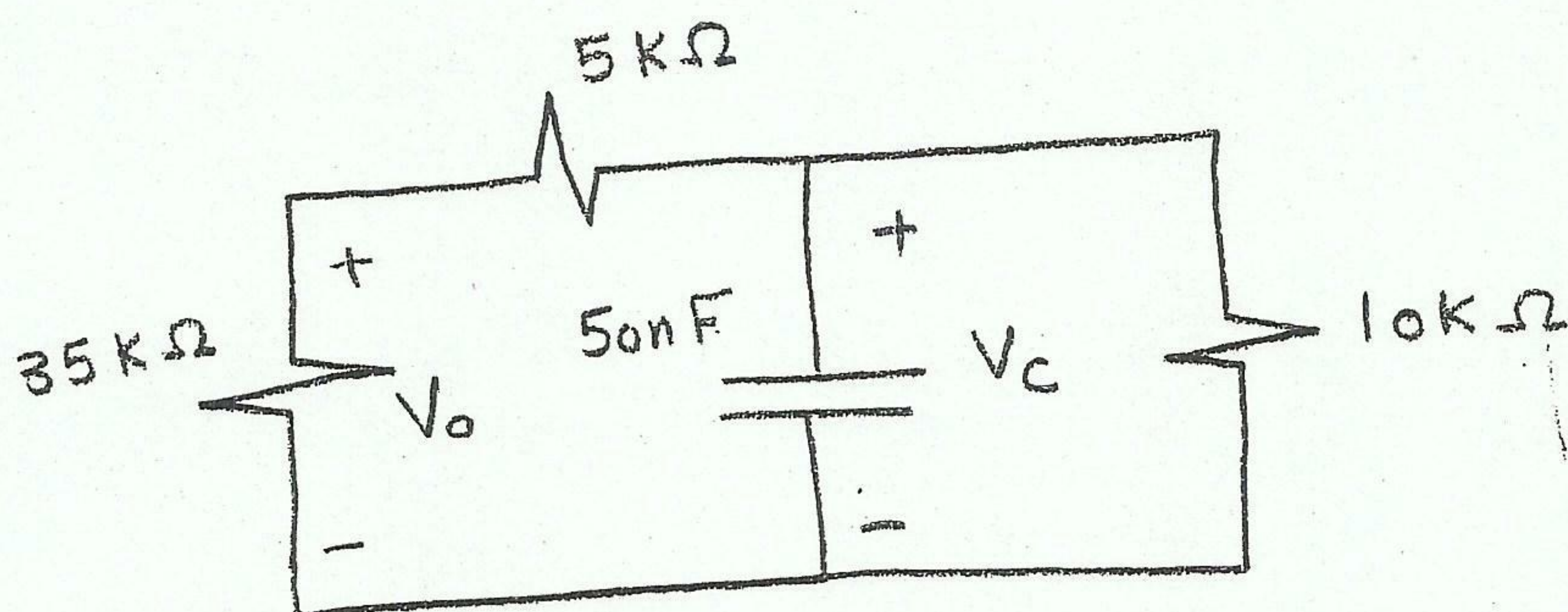

$$\tau = 400 \mu s \quad , \quad \frac{1}{\tau} = 2500 \text{ s}^{-1}$$

$$\therefore V_c(t) = 12.5 e^{-2500(t - 1.4 \times 10^{-3})} \text{ V}$$

$$\therefore V_c(1.6 \text{ ms}) = 12.5 e^{-2500(1.6 - 1.4) \times 10^{-3}} = 7.58 \text{ V}$$

$$\therefore V_o(1.6 \text{ ms}) = 7.58 \times \frac{35}{35 + 5} = 6.63 \text{ V}$$